
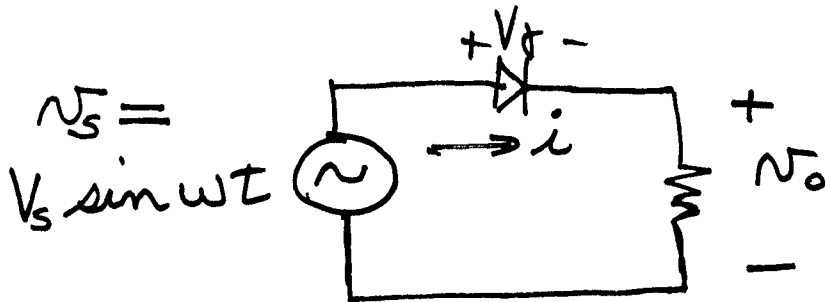


DIODE APPLICATIONS


RECTIFIERS

AC TO DC CONVERTER

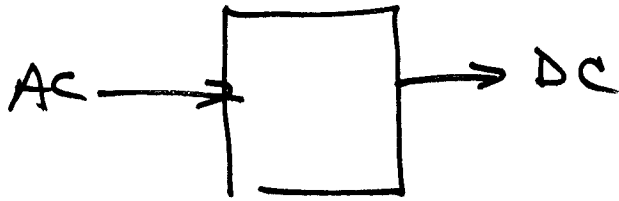

① IDEAL DIODE


DIODE is ON for $V_s > 0$

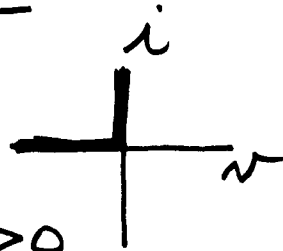

$$V_f = 0 \quad V_r = 0$$

$$V_o = V_s = V_s \sin \omega t$$



DIODE OFF, $V_s < 0$, $V_o = 0$



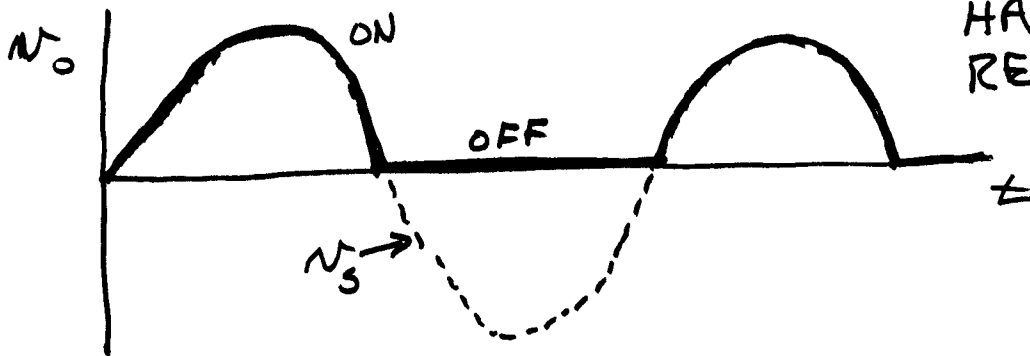


HALF-WAVE RECTIFIER

② V_f DIODE ON for $V_s > V_f$

$$V_o = V_s - V_f$$

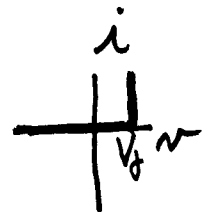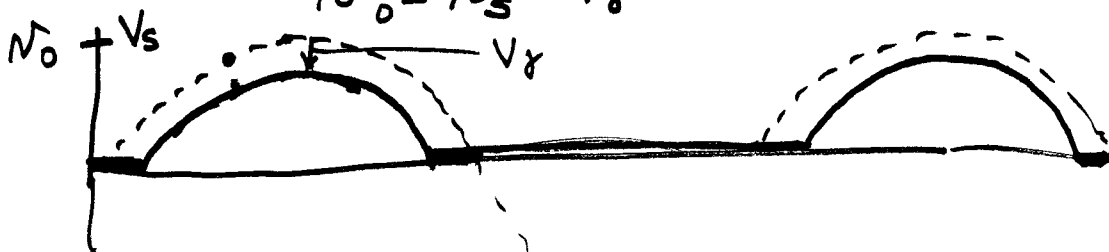

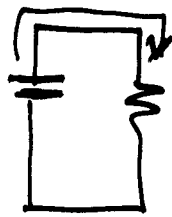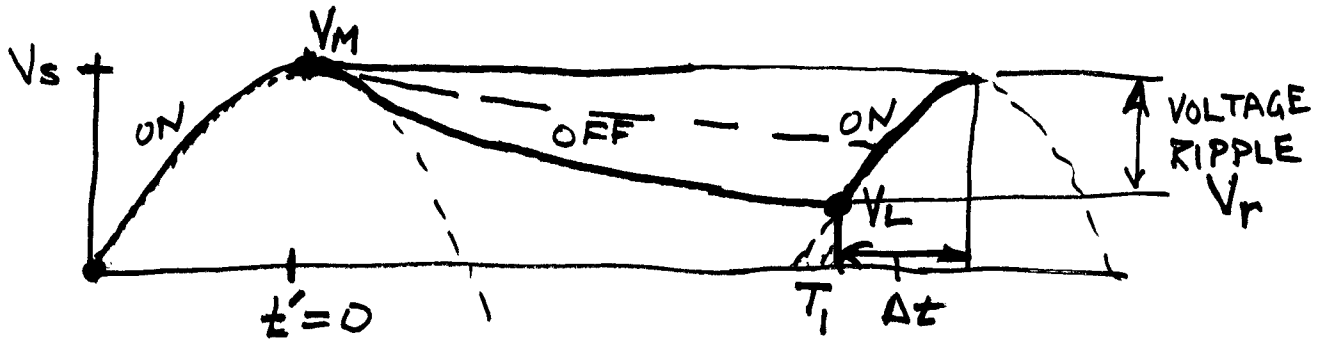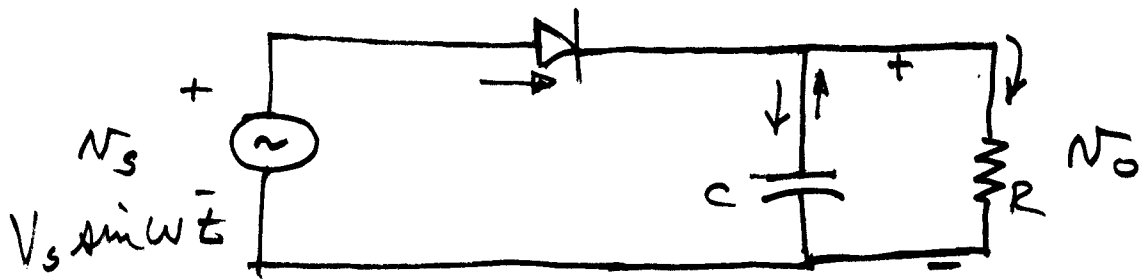

$$V_o = V_L e^{-t/RC}$$

I.C. $RC = \tau$

$$V_o = V_M e^{-t/RC}$$

$$V_L = V_M e^{-T_1/RC}$$

DESIGN FOR $T_1 \ll RC$ (SMALL DECAY)
(SMALL V_r)

$$e^x \approx 1 + x + \frac{x^2}{2} \dots$$


$$e^{-T_1/RC} \approx 1 - \frac{T_1}{RC}$$

$$V_r = V_M - V_L = V_M - V_M e^{-T_1/RC} \approx V_M (1 - e^{-T_1/RC})$$

$$V_r \approx V_M \left[1 - \left(1 - \frac{T_1}{RC} \right) \right] = V_M \left(\frac{T_1}{RC} \right) \approx V_M \left(\frac{T}{RC} \right)$$

$$T = \frac{1}{f}$$

$$V_r \approx \frac{V_M}{RCf}$$

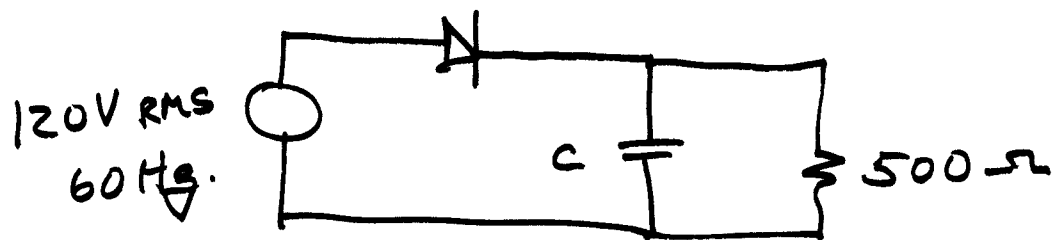

FIND C SUCH THAT $V_r = 0.01 V_M$
1% RIPPLE

$$C = \frac{V_M}{R f V_r} = \frac{V_M}{R f (0.01 V_M)} =$$

$$C = \frac{1}{(500)(60)(0.01)} = 3333 \mu F$$