

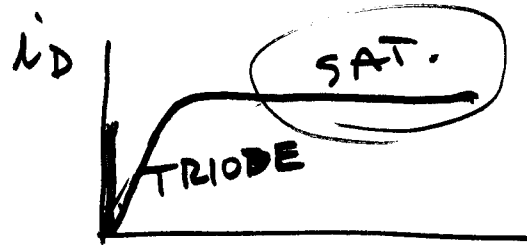


# MOSFET DIFFERENTIAL AMP.

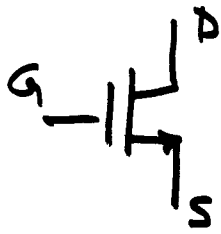

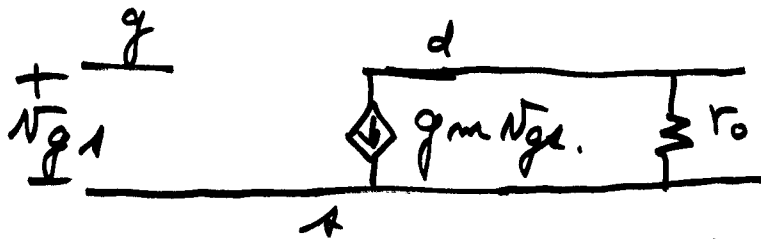
$$i_D = K_m (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$$




$$r_o = \frac{V_A}{I_{DQ}} = \frac{1}{\lambda I_{DQ}}$$

$$g_m = 2\sqrt{K_m I_{DQ}}$$
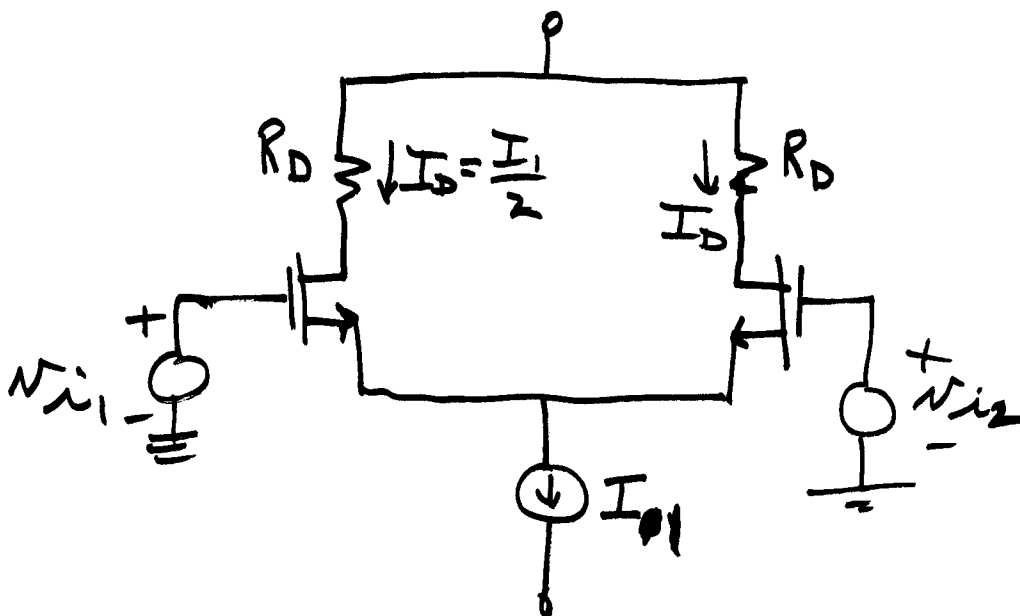
$$K_m = \left(\frac{W}{L}\right) \frac{k'_m}{2}$$



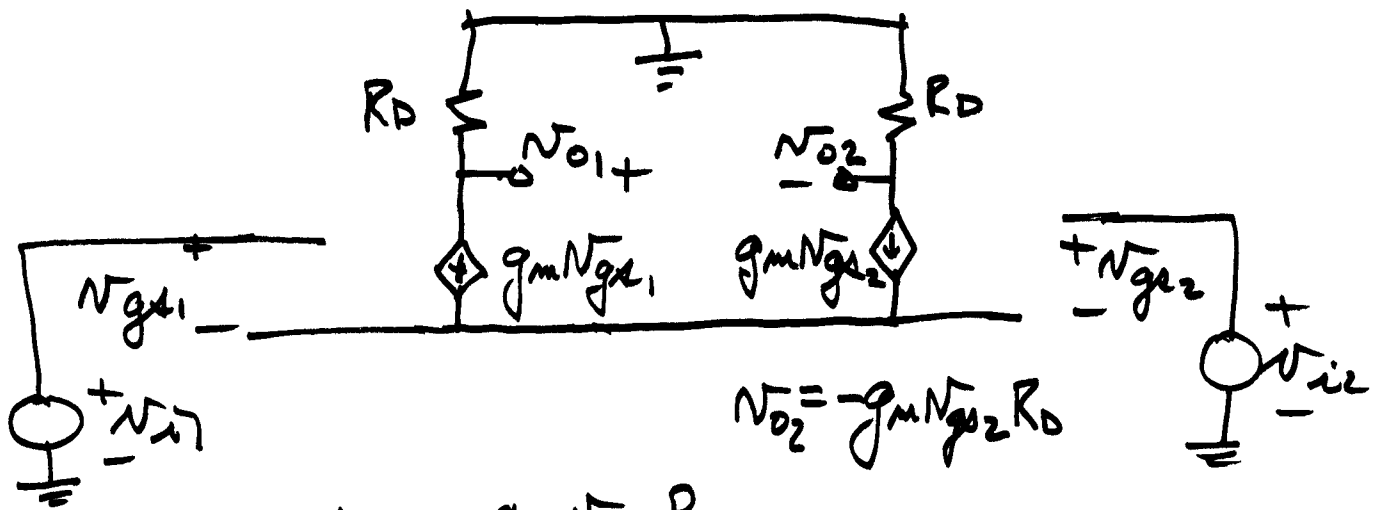

$$N_{o1} = -g_m N_{gs1} R_D$$

$$\begin{aligned} N_{o1} - N_{o2} &= -g_m N_{gs1} R_D + g_m N_{gs2} R_D \\ &= -g_m R_D (N_{gs1} - N_{gs2}) \end{aligned}$$

$$-N_{i1} + N_{gs1} - N_{gs2} + N_{i2} = 0$$


$$N_{gs1} - N_{gs2} = N_{i1} - N_{i2}$$

$$\boxed{\frac{N_{o1} - N_{o2}}{N_{i1} - N_{i2}} = -g_m R_D}$$

$$K_m = 0.1 \text{ mA/V}^2$$

$$= 100 \mu\text{A/V}^2$$

$$V_T = 1 \text{ V.}$$

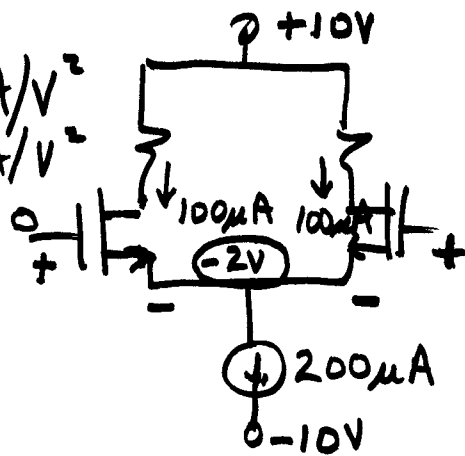

$$I_D = K_m (V_{GS} - V_{TN})^2$$

$$V_{GS} = \sqrt{\frac{I_D}{K_m}} + V_{TN}$$

$$V_{GS} = \sqrt{\frac{100 \mu}{100 \mu}} + 1$$

$$V_{GS} = 2 \text{ V}$$

For saturation

$$V_{DS} > V_{GS} - V_T = 2 - 1 = 1 \text{ V.}$$

LET  $V_{DS} = 4 \text{ V.} \Rightarrow V_D = 2 \text{ V.}$

$$V_D = 10 - I_D R_D = 2$$

$$I_D R_D = 8 \text{ V.}$$

$$R_D = \frac{8 \text{ V}}{100 \mu\text{A}} = 80 \text{ K}$$

$$g_m = 2 \sqrt{K_m I_D} = 2 \sqrt{100 \mu \cdot 100 \mu} = 200 \mu\text{A/V}$$

.2 mA/V

$$A_v = -g_m R_D = -(0.2 \text{ m})(80 \text{ K})$$

$$= -16$$

---

CURRENT MIRROR - NEXT CLASS