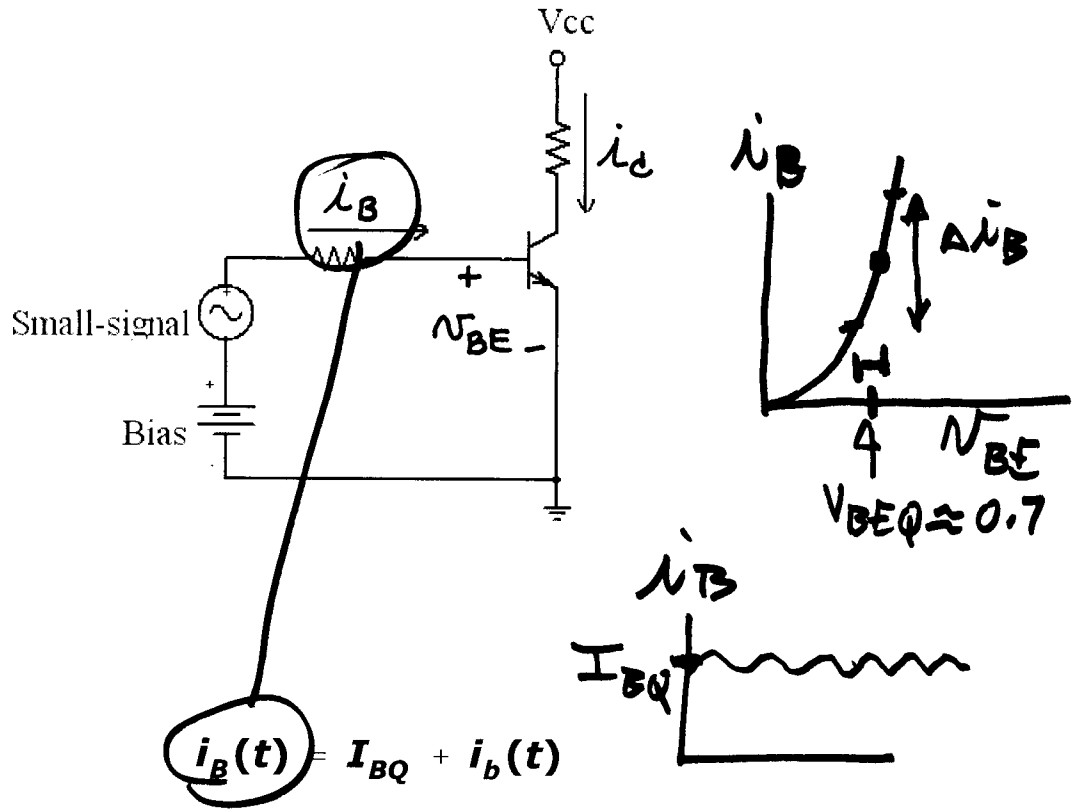


BJT SMALL-SIGNAL MODEL



$$i_c = I_S \left[e^{v_{BE}/V_T} - 1 \right] \approx I_S \left[e^{v_{BE}/V_T} \right]$$

$$i_B = \frac{i_c}{\beta} = \frac{I_S}{\beta} e^{v_{BE}/V_T} \quad \text{TOTAL}$$

$$v_{BE} = V_{BEQ} + v_{be}(t) \quad \approx 0.7$$

$$I_{BQ} + i_b(t) = \frac{I_S}{\beta} e^{[V_{BEQ} + v_{be}(t)]/V_T}$$

$$I_{BQ} + i_b(t) = I_{BQ} \left[e^{v_{be}(t)/V_T} \right]$$

$$I_{BQ} + i_b(t) = \frac{I_S}{\beta} \left[e^{V_{BEQ}/V_T} \right] \left[e^{v_{be}(t)/V_T} \right] = I_{BQ} e^{v_{be}(t)/V_T}$$

$$e^x \approx 1 + x \quad \text{for } x \ll 1$$

$$I_{BQ} + i_b(t) \approx I_{BQ} \left[1 + \frac{v_{be}(t)}{V_T} \right] = I_{BQ} + I_{BQ} \frac{v_{be}(t)}{V_T}$$

$$i_b(t) = I_{BQ} \left[\frac{v_{be}(t)}{V_T} \right] = v_{be}(t) \left[\frac{I_{BQ}}{V_T} \right]$$

$$\frac{v_{be}(t)}{i_b(t)} = \left[\frac{V_T}{I_{BQ}} \right] = r_{\pi}$$


r_{π} is the small-signal resistance, also called the diffusion resistance. It gives the relationship between small-signal voltage and small-signal current.

$$r_{\pi} = \left[\frac{V_T}{I_{BQ}} \right] = \left[\frac{\beta V_T}{I_{CQ}} \right]$$



$$i_c(t) = \beta i_b(t) = \beta \frac{v_{be}(t)}{r_{\pi}}$$

$$g_m = \frac{i_c(t)}{v_{be}(t)} = \frac{\beta}{r_{\pi}} = \frac{I_{CQ}}{V_T}$$

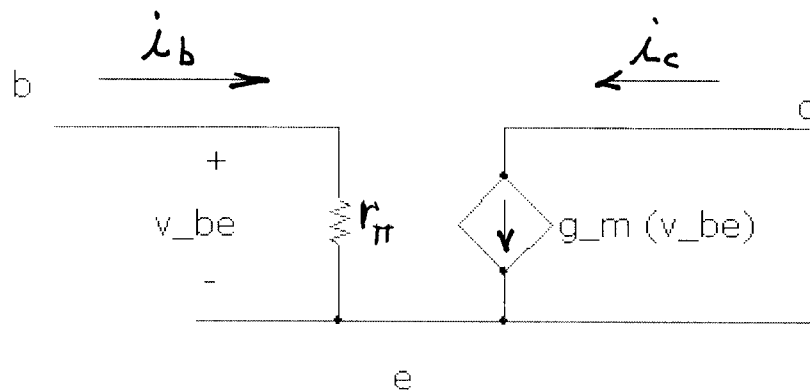g_m is the transconductance. It gives the relationship between the small-signal collector current and a small-signal base-emitter voltage.



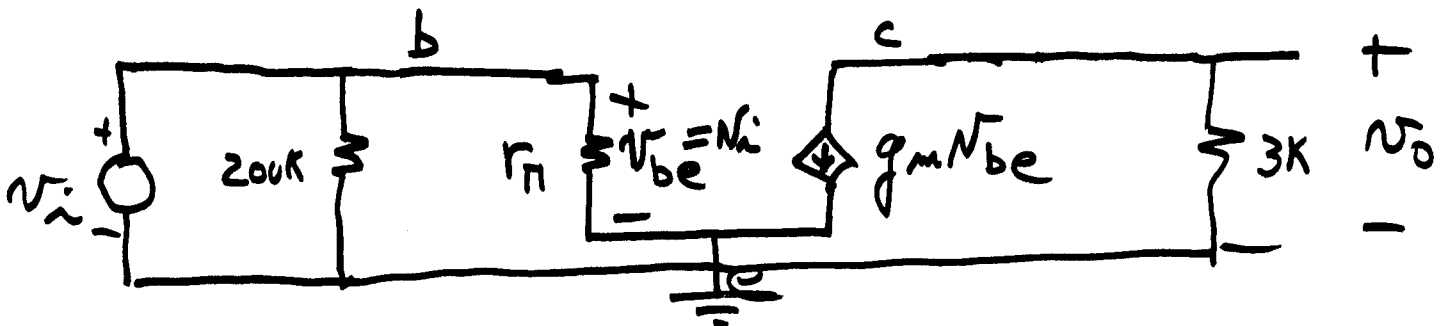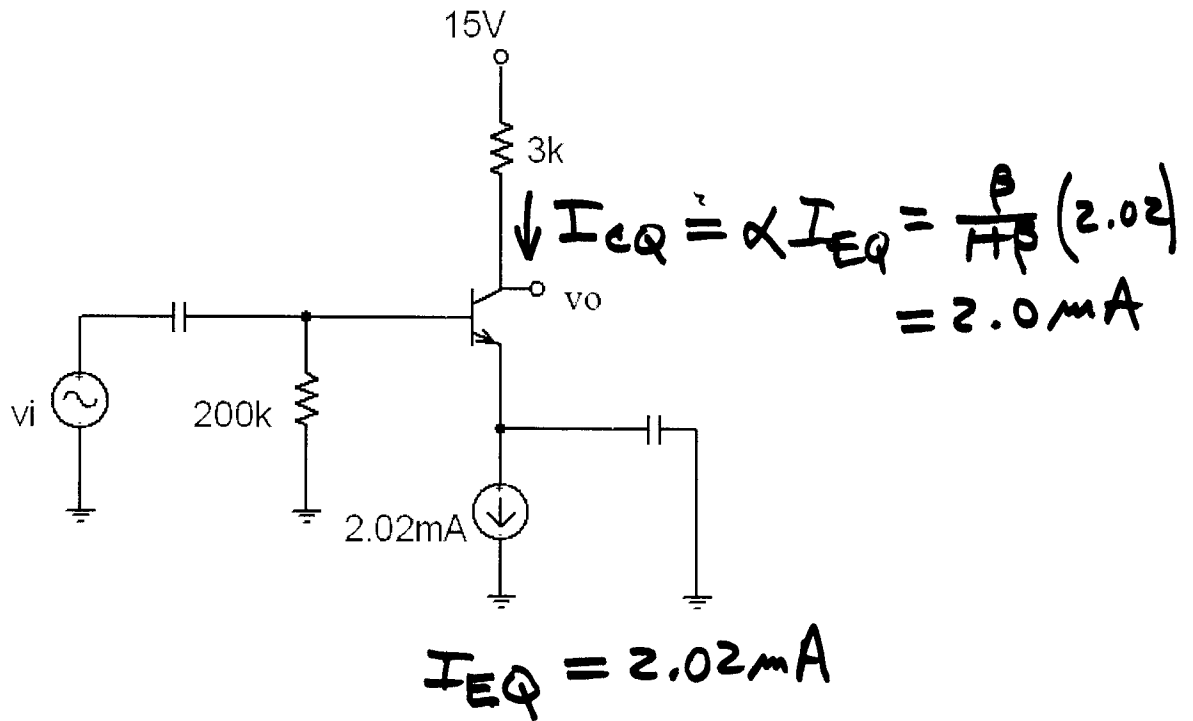Determine the gain $v_o(t)/v_i(t)$. $\beta = 100$



$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(26 \text{ mV})}{2 \text{ mA}} = 1300 \Omega = 1.3 \text{ k}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{2 \text{ mA}}{26 \text{ mV}} = 0.077 \text{ A/V} = 77 \text{ mA/V}$$

$$v_o = -g_m v_{be} (3 \text{ k}) = -g_m v_i (3 \text{ k})$$

$$\frac{v_o}{v_i} = -g_m 3 \text{ k} = (-77)(3) = -231$$