
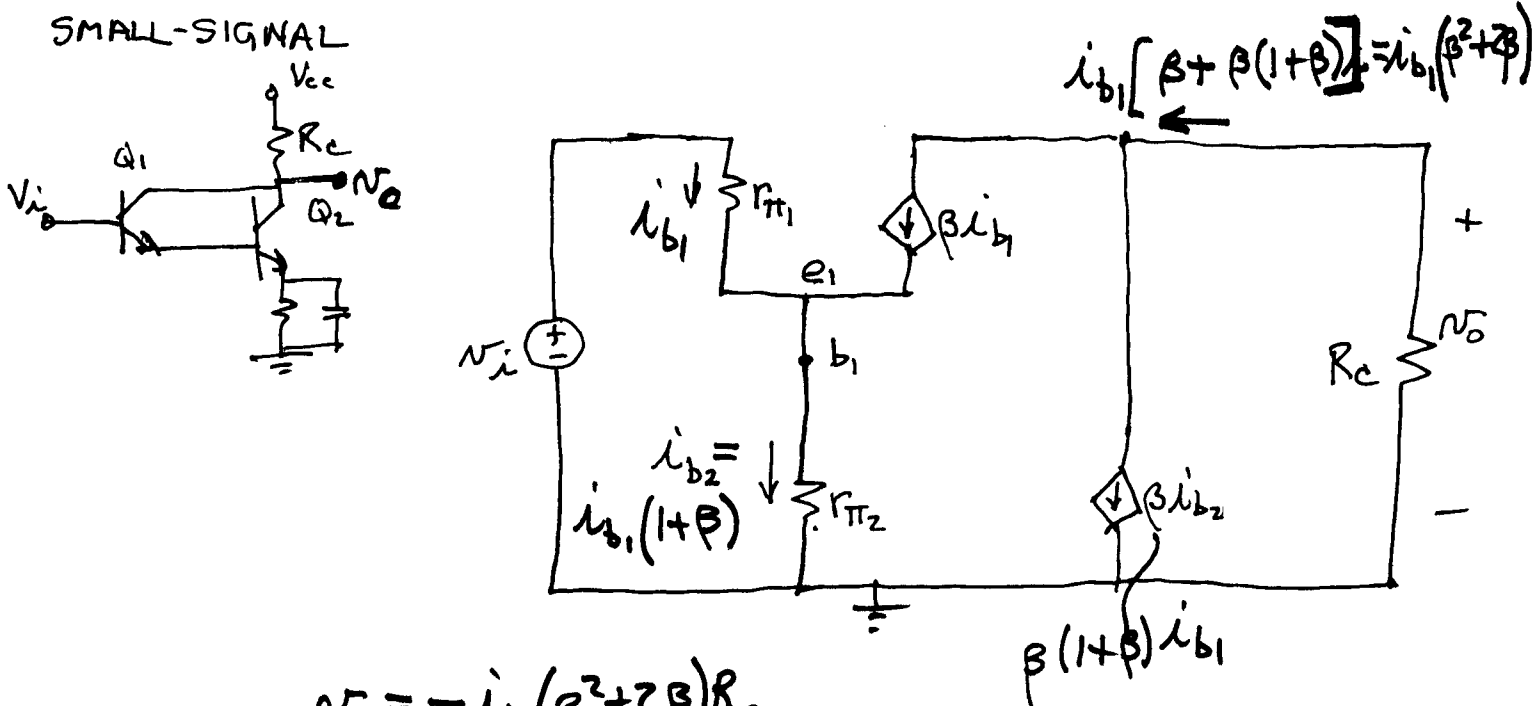


DARLINGTON CONFIGURATION

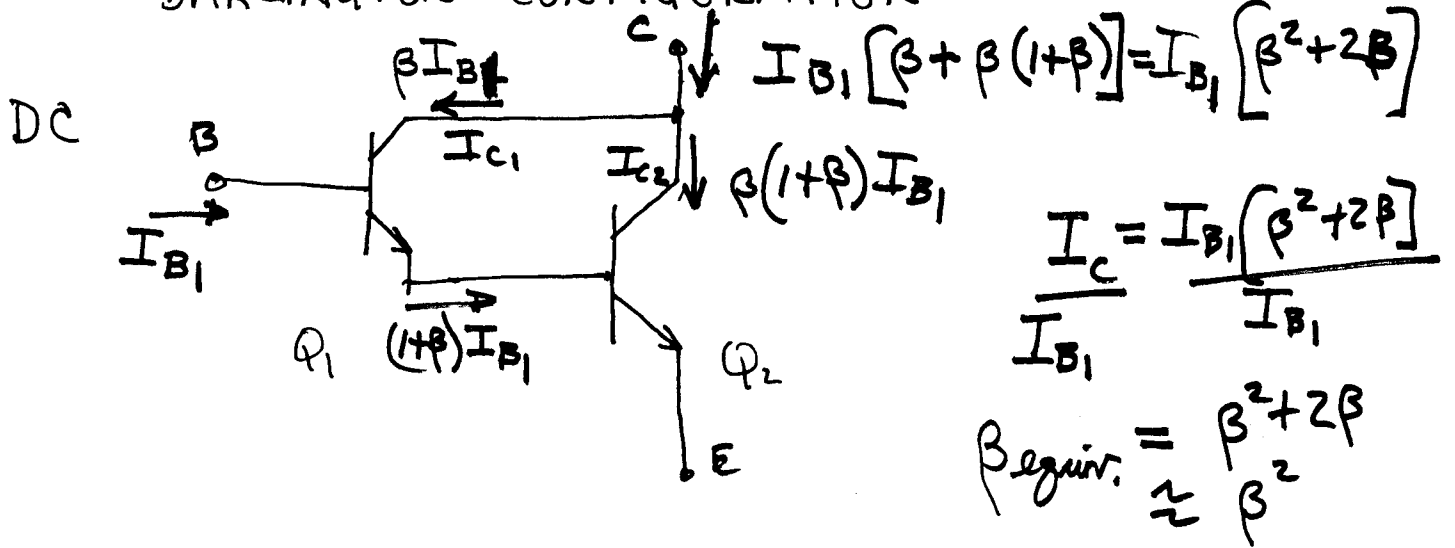

$$v_o = -i_{b1} (\beta^2 + 2\beta) R_c$$

$$v_i = i_{b1} r_{\pi 1} + i_{b1} (1 + \beta) r_{\pi 2}$$

$$A_w = \frac{v_o}{v_i} = - \frac{(\beta^2 + 2\beta) R_c}{r_{\pi 1} + (1 + \beta) r_{\pi 2}} = - \frac{(\beta^2 + 2\beta) R_c}{2(1 + \beta) r_{\pi 2}}$$

$$H_{c1} = \frac{I_{c2}}{I_{b1}}$$

$$r_{\pi 1} = \frac{\beta V_T}{I_{c1}}$$

$$r_{\pi 2} = \frac{\beta V_T}{I_{c2}}$$

$$r_{\pi 1} = \frac{\beta V_T}{I_{c2} / (1 + \beta)} = (1 + \beta) \frac{\beta V_T}{I_{c2}} = (1 + \beta) r_{\pi 2}$$

$$A_N = \frac{N_o}{N_i} = - \frac{\beta^2 R_c}{2\beta r_{\pi 2}} = - \frac{\beta R_c}{2r_{\pi 2}}$$

$$r_{\pi 2} = \frac{\beta V_T}{I_{c2}}$$

$$A_N = - \frac{\beta R_c}{2 \left[\frac{\beta V_T}{I_{c2}} \right]} = - \frac{I_{c2} R_c}{2V_T}$$

$$A_N = \frac{N_o}{N_i} \approx - \frac{I_c R_c}{2V_T} \quad \text{DARLINGTON}$$