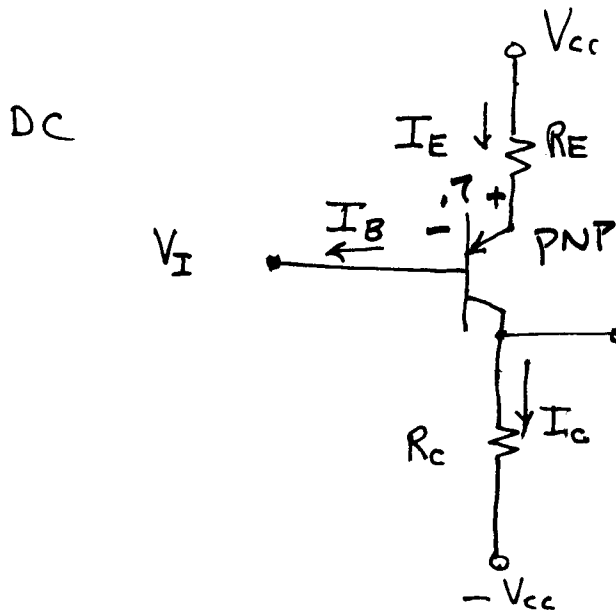


ALTERNATIVE LEVEL SHIFTER




$$V_{cc} = I_E R_E + 0.7 + V_E$$

$$I_E = \frac{V_{cc} - 0.7 - V_E}{R_E}$$

$$V_o = I_c R_c - V_{cc}$$

$$I_c = \alpha I_E$$

SMALL-SIGNAL

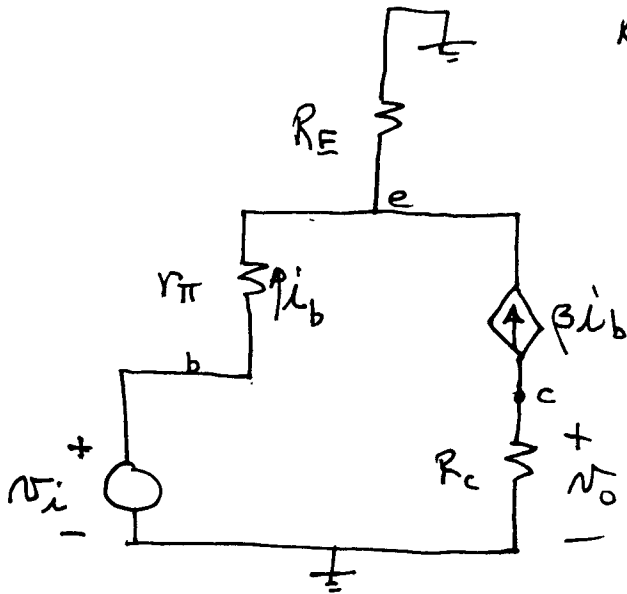

$$\text{KVL: } v_i = i_b r_{\pi} + (\beta + 1) i_b R_E$$

$$v_o = -\beta i_b R_c$$

$$\frac{v_o}{v_i} = \frac{-\beta R_c}{r_{\pi} + (\beta + 1) R_E}$$

$$\text{if } (\beta + 1) R_E \gg r_{\pi}, \frac{v_o}{v_i} = -\frac{\beta R_c}{(\beta + 1) R_E} \approx -\frac{R_c}{R_E}$$

$$\frac{v_o}{v_i} \approx -\frac{R_c}{R_E}$$