

$$\beta = \frac{1 - \alpha}{\alpha} \quad \alpha = \frac{\beta}{1 + \beta}$$

$$i_C = \alpha i_E$$

$$i_E = (1 + \beta i_B)$$


$$i_C = \beta i_B$$

$$i_E = i_C + i_B \quad \text{(KCL)}$$


$$i_C \approx I_S e^{v_{BE}/V_T}$$

$$I_C \left( e^{v_{BE}/V_T} - 1 \right)$$
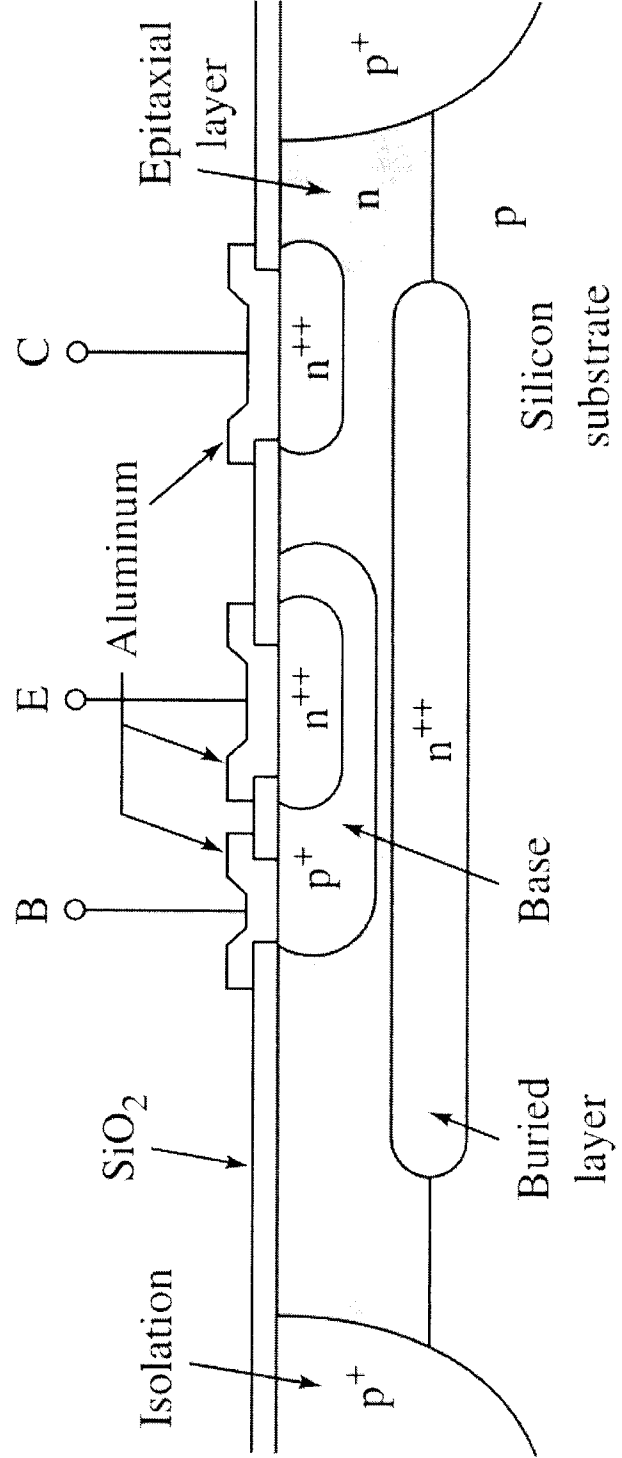
# Cross Section of Integrated Circuit nnp Transistor



## ANALYSIS OF THE DC BIAS CIRCUIT

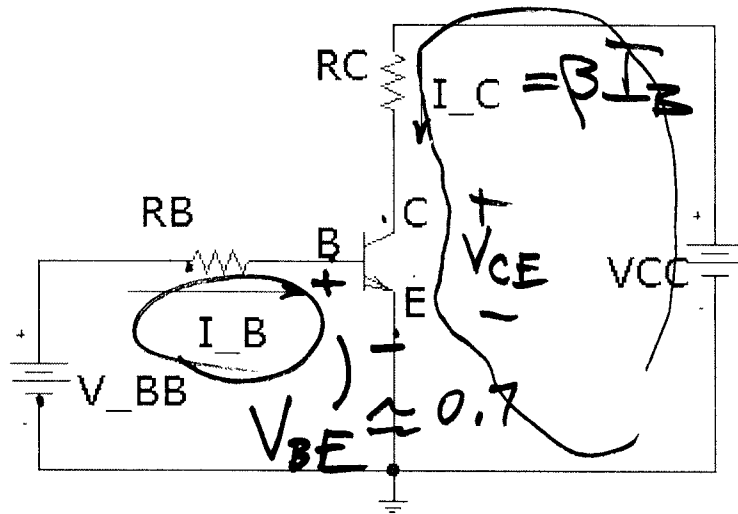

KVL on the base side:

$$-V_{BB} + I_B R_B + V_{BE} = 0$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$\underline{I_B} = \frac{V_{BB} - 0.7}{R_B}$$

KVL on the collector side:


$$-V_{CC} + I_C R_C + V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$\boxed{I_C = \beta I_B}$$

## Example:

$$\beta = 100$$


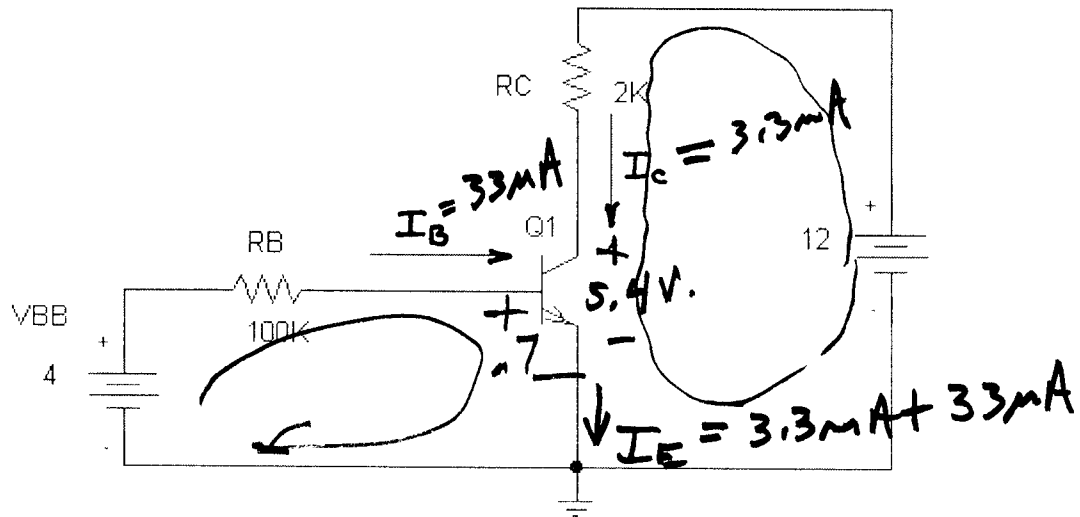


$$I_B = \frac{V_{BB} - 0.7}{R_B} = \frac{4 - 0.7}{100k} = 33 \mu A$$



$$I_C = \beta I_B = 100(33 \mu A) = 3.3 mA$$

$$V_{CE} = V_{CC} - I_C R_C = 12 - (3.3)(2) = 5.4 V.$$

# BJT BIASING WITH A SINGLE DC SOURCE

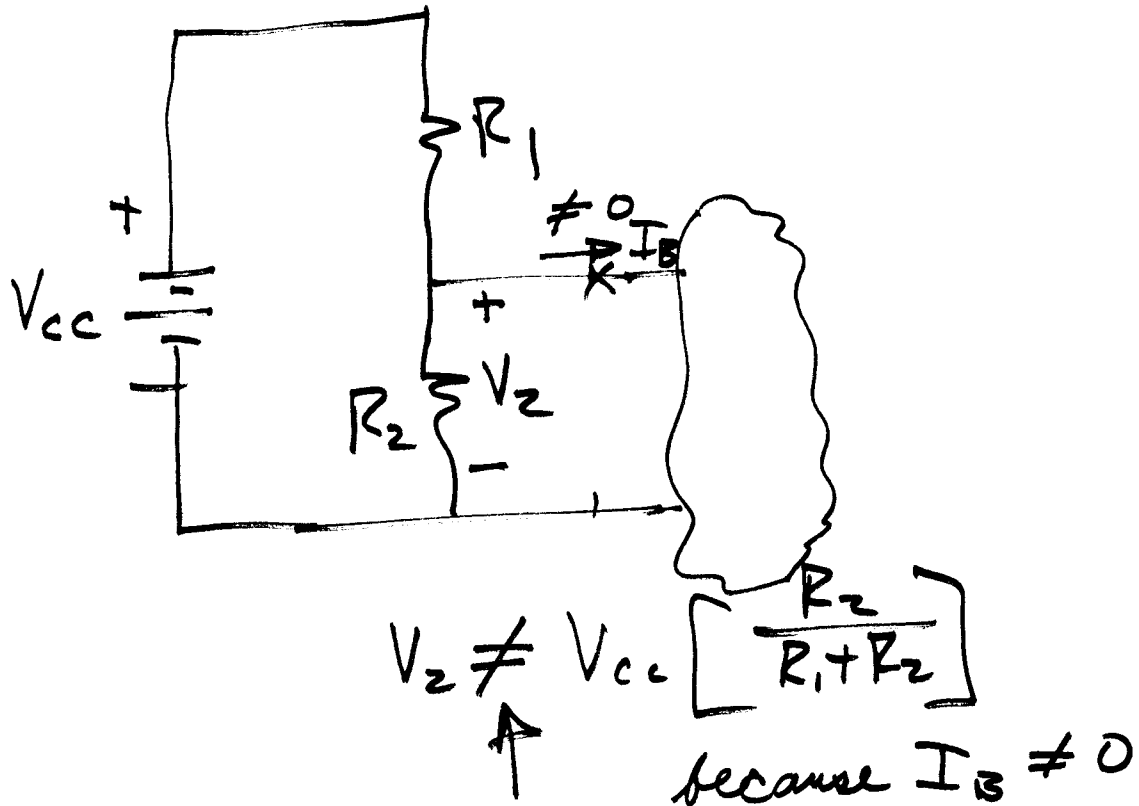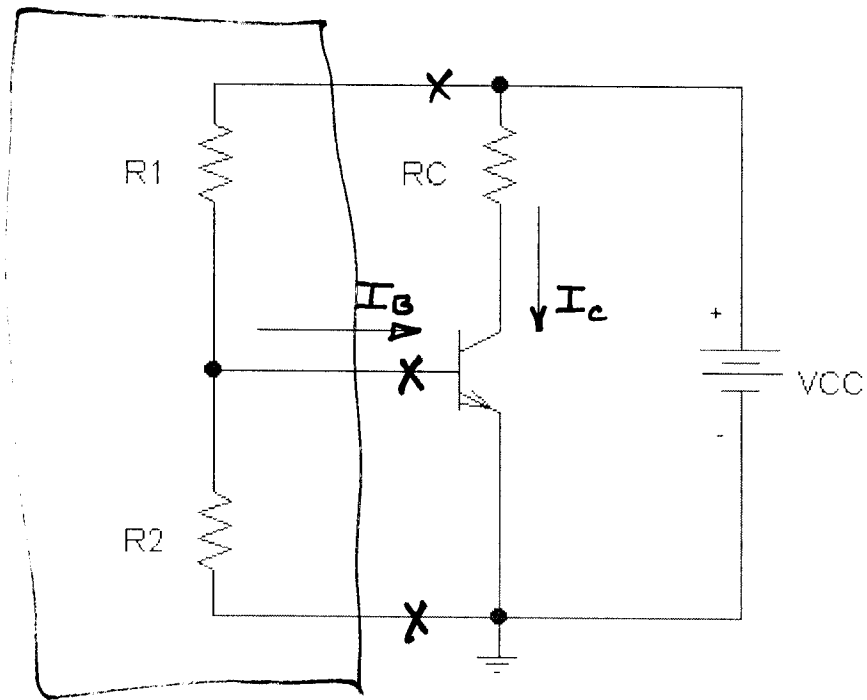

# Thevenin Equivalent on the Base Side:

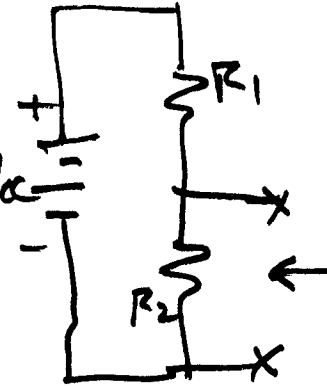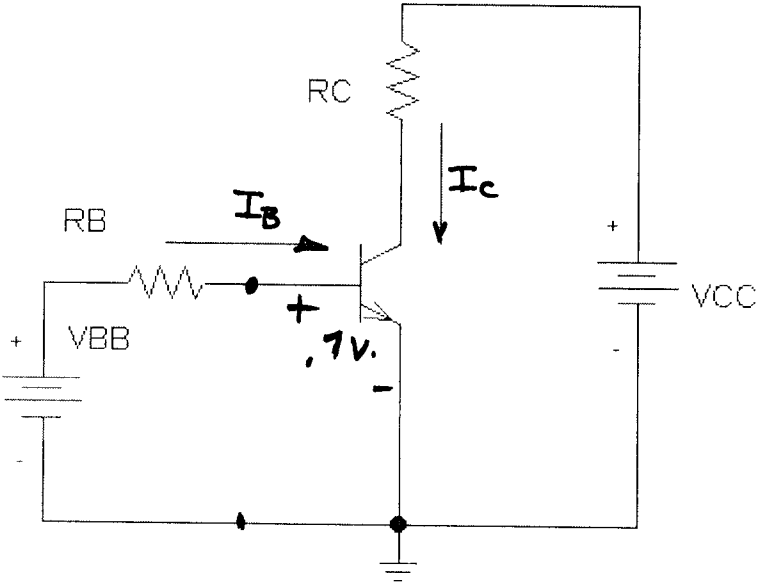


← THEV. EQ.

$$V_{BB} = V_{th} = V_{CC} \left( \frac{R_2}{R_1 + R_2} \right)$$

$$R_B = R_{th} = \left( \frac{R_1 R_2}{R_1 + R_2} \right)$$

## Biassing with $R_E$

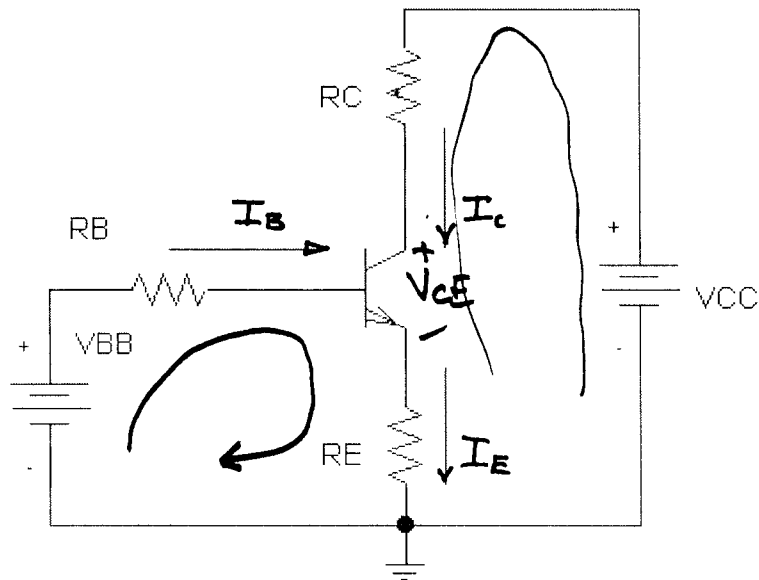

KVL on the base side:

$$-V_{BB} + I_B R_B + V_{BE} + I_E R_E = 0$$

*0.7V.*

$$I_E = I_C + I_B = I_B (\beta + 1)$$

$$I_C = \beta I_B$$

$$-V_{BB} + I_B R_B + V_{BE} + I_B(\beta + 1)R_E = 0$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B + (\beta + 1)R_E}$$

$$I_C = \beta I_B$$

KVL

$$-V_{CC} + I_C R_C + V_{CE} + I_E R_E = 0$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

Why do we include  $R_E$ ?

$$I_B = \frac{V_{BB} - V_{BE}}{R_B + (\beta + 1)R_E}$$

$$\begin{aligned} R_E &= 0 \\ I_B &= \frac{V_{BB} - V_{BE}}{R_B} \\ I_C &= \beta I_B \end{aligned}$$


$$I_C = \beta I_B = \beta \left( \frac{V_{BB} - V_{BE}}{R_B + (\beta + 1)R_E} \right)$$

If we make  $(\beta + 1)R_E \gg R_B$ ,

$$I_C = \beta \left( \frac{V_{BB} - V_{BE}}{R_B + (\beta + 1)R_E} \right) \approx \beta \left( \frac{V_{BB} - V_{BE}}{(\beta + 1)R_E} \right)$$

$$I_C = \left( \frac{V_{BB} - V_{BE}}{R_E} \right) \left[ \frac{\beta}{\beta + 1} \right] \approx \frac{V_{BB} - V_{BE}}{R_E}$$

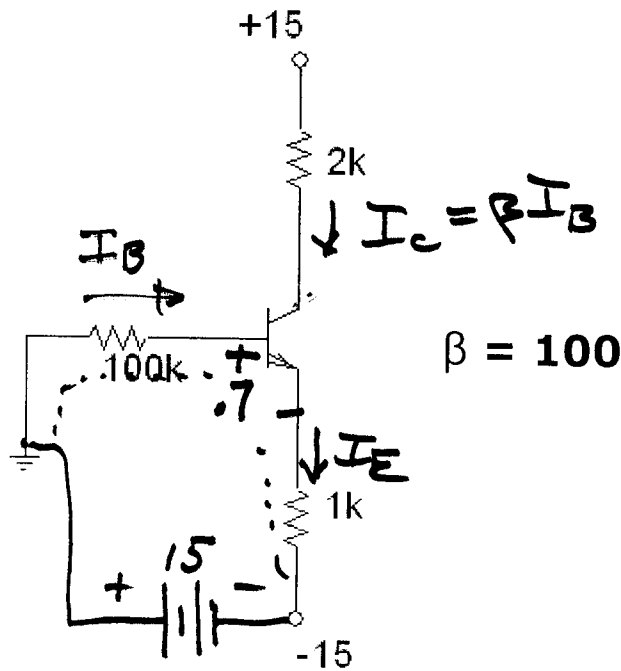$\therefore I_C$  is nearly independent of  $\beta$ .



① SOLVE FOR  $I_B$

$$100k I_B + 0.7 + I_E(1k) - 15 = 0$$

$$I_B = \frac{I_E}{\beta + 1}$$

$$\left[ \frac{I_E}{\beta + 1} \right] 100k + I_E(1k) = 14.3$$

$$I_E = 7.19 \text{ mA}$$

$$I_B = \frac{I_E}{\beta + 1} = 71.1 \mu\text{A}$$

$$I_C = \beta I_B = 7.11 \text{ mA}$$

$$V_{CE} = 30 - I_C(2k) - I_E(1k) = 8.58 \text{ V}$$

