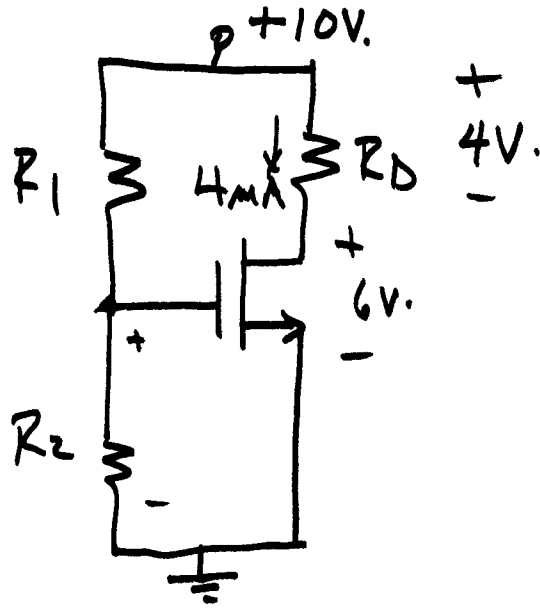


TEST FRIDAY, SEPT 22



in SATURATION:

$$V_{DS} \geq V_{GS} - V_{TN}$$

DESIGN FOR

$$I_D = 4mA$$

$$V_{DS} = 6V$$

GIVEN $K_M = 2mA/V^2$

$$V_{TN} = 2V$$

DETERMINE

$$R_D, R_1, R_2$$

$$I_D = K_M (V_{GS} - V_{TN})^2$$

$$R_D = 1K$$

$$(V_{GS} - V_{TN})^2 = \frac{I_D}{K_M}$$

$$V_{GS} - V_{TN} = \sqrt{\frac{I_D}{K_M}}$$

$$V_{GS} = \sqrt{\frac{I_D}{K_M}} + V_{TN}$$

$$V_{GS} = \sqrt{\frac{4mA}{2mA}} + 2 = \sqrt{2} + 2 \approx 3.4V$$

$$V_{GS} = 10 \left(\frac{R_2}{R_1 + R_2} \right) = 3.4$$

$$\frac{R_1 + R_2}{R_2} = \frac{10}{3.4}$$

$$\Rightarrow \frac{R_1}{R_2} + 1 = \frac{10}{3.4}$$


$$\frac{R_1}{R_2} = \frac{10}{3.4} - 1 = 1.94$$

$$R_2 = 1M\Omega$$

$$R_1 = 1.94M\Omega$$

DC VALUES = BIAS VALUES

NMOS
PMOS

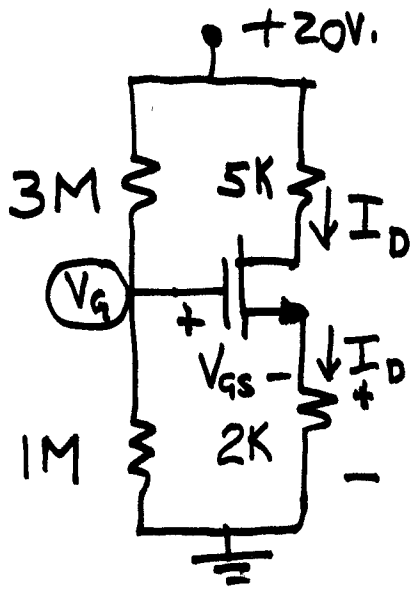

$$K_M = 1 \text{ mA/V}^2$$

$$V_{TN} = 2 \text{ V.}$$

$$I_D = K_M (V_{GS} - V_{TN})^2$$

$$V_{GS} = V_G - V_S$$

$$V_G = 20 \left(\frac{1}{1+3} \right) = 5 \text{ V.} \quad \left. \vphantom{V_G} \right\} V_{GS} = 5 - 2K I_D$$

$$V_S = 2K I_D$$

$$I_D = 1 (5 - 2I_D - 2)^2 = (3 - 2I_D)^2$$

$$I_D = 9 - 12I_D + 4I_D^2$$

$$4I_D^2 - 13I_D + 9 = 0 \Rightarrow \begin{matrix} I_D = 2.25 \text{ mA} \\ I_D = 1 \text{ mA} \end{matrix}$$

IF $I_D = 1 \text{ mA}$ $V_{GS} = 5 - 2 = 3 \text{ V.}$

IF $I_D = 2.25 \text{ mA}$ $V_{GS} = 5 - 2(2.25) = 0.5 \text{ V.}$

