

Small-signal equivalent circuits for MOSFET amplifiers.


Notation: voltages and currents contain a DC component and a small-signal component.

Small-signal means a time-varying voltage or current that is small in amplitude.


The total voltage or current is the sum of the DC and small-signal components.

total = DC + small-signal i_D

$$i_D(t) = I_{DQ} + i_d(t)$$

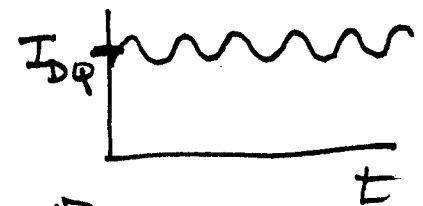

$$v_{GS}(t) = V_{GSQ} + v_{gs}(t)$$

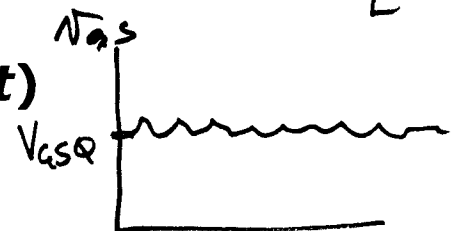

MOSFET amplifiers always operate with the MOSFET in saturation.

$$\underbrace{i_D}_{\text{Total}} = K_n \left(\underbrace{v_{GS}}_{\text{Total}} - V_{TN} \right)^2$$

$$I_{DQ} + i_d(t) = K \left(V_{GS} + v_{gs}(t) - V_{TN} \right)^2$$

$$i_D = K_n (v_{GS} - V_{TN})^2$$

$$\begin{aligned}
 I_{DQ} + i_d(t) &= K_n (\overbrace{V_{GS}}^{\text{DC}} + v_{gs}(t) - \overbrace{V_{TN}}^{\text{"DC"}})^2 \\
 &= K_n [(V_{GS} - V_{TN}) + v_{gs}(t)]^2 \\
 &= \underbrace{K_n (V_{GS} - V_{TN})^2}_{I_{DQ}} + \underbrace{2K_n (V_{GS} - V_{TN}) v_{gs}(t)}_{i_d(t)} + \underbrace{K_n v_{gs}^2}_{\approx 0}
 \end{aligned}$$

DC term + small-signal + very small

Neglect the very small term. Then,


$$i_d(t) \approx \left[2K_n (V_{GSQ} - V_{TN}) \right] v_{gs}(t)$$

$$g_m = 2K_n (V_{GSQ} - V_{TN})$$

$$i_d(t) = g_m v_{gs}(t)$$

g_m is called the *transconductance*

SMALL-SIGNAL EQUIVALENT CIRCUIT

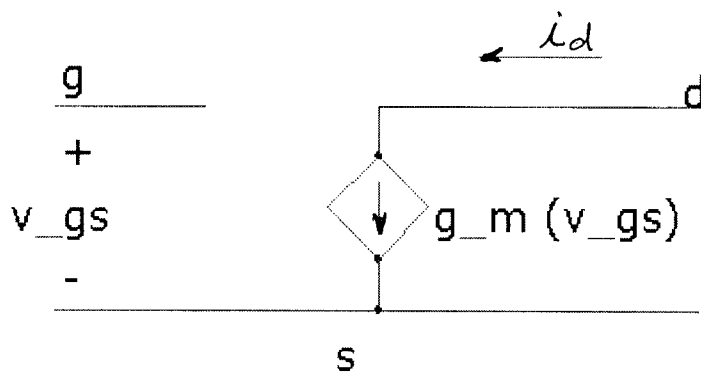

MODEL FOR
THE MOSFET
SMALL-SIGNAL
COMPONENT

v_{gs} is the time-varying portion of the gate-to-source voltage. i_d is the resulting time-varying portion of the drain current.

$$g_m = 2K_n (V_{GSQ} - V_{TN})$$


$$I_{DQ} = K_n (V_{GSQ} - V_{TN})^2$$

$$(V_{GSQ} - V_{TN}) = \sqrt{\frac{I_{DQ}}{K_n}}$$

$$\therefore g_m = 2\sqrt{K_n I_{DQ}}$$

$$K_n = \left(\frac{W}{L} \right) \frac{k'_n}{2}$$

$$k'_n = \mu_n C_{ox}$$

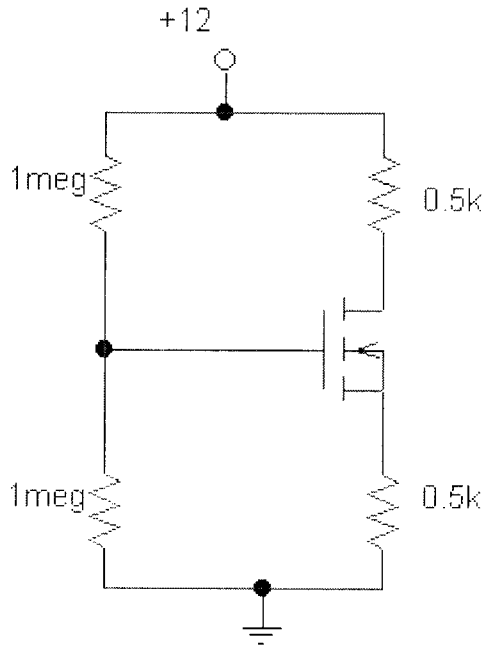


SOLVE FOR:

$$\left. \begin{aligned} I_{DQ} &= 6 \text{ mA} \\ V_{GSQ} &= 3 \text{ V.} \end{aligned} \right\}$$


$$K_n = 1.5 \text{ mA/V}^2$$

$$g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{1.5(6)} = 6 \text{ mA/V}$$


TOTAL

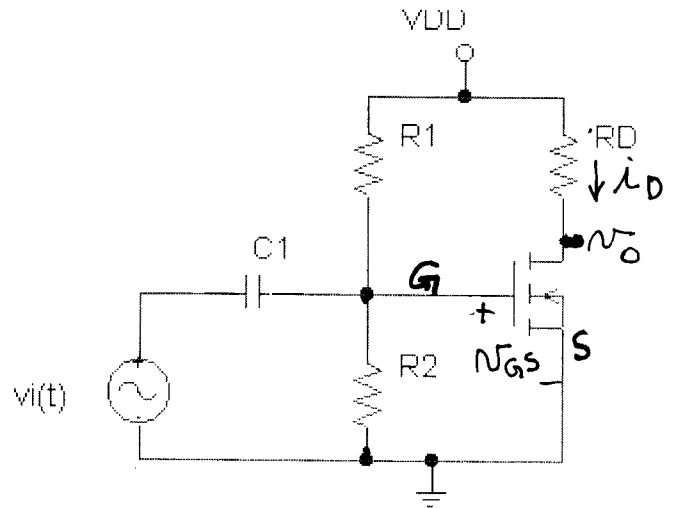


DC ONLY

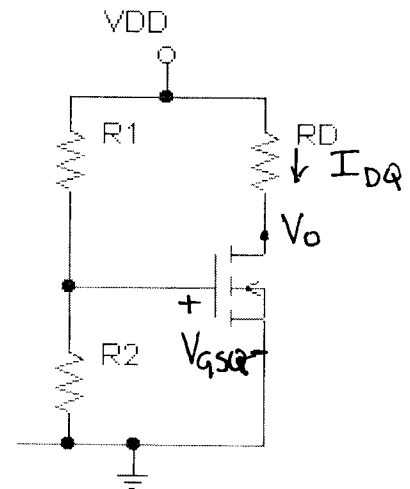

SMALL-SIGNAL ONLY

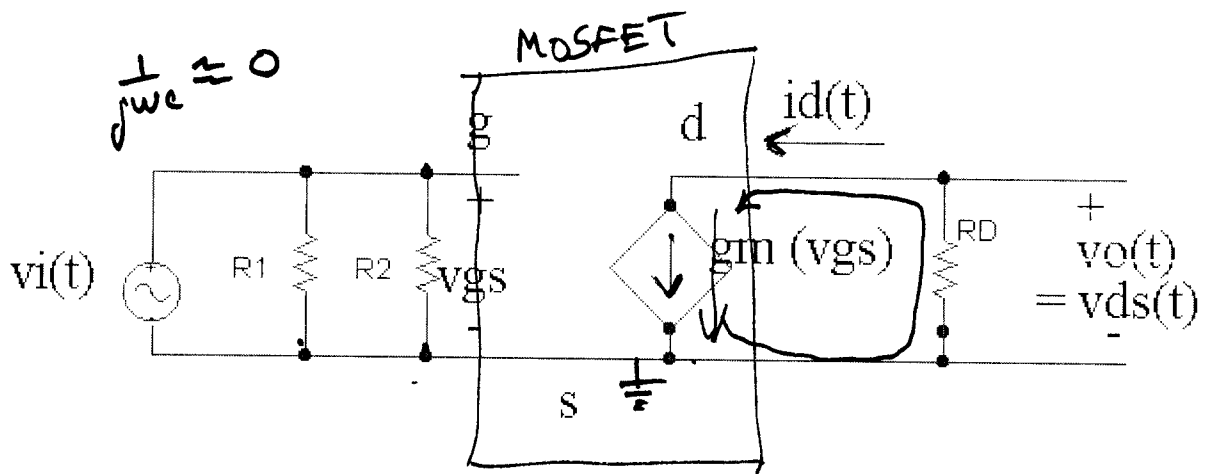

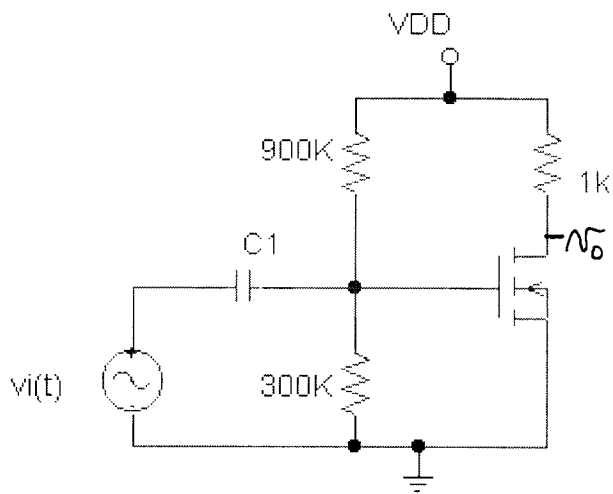


$$I_{DQ} = 6 \text{ mA}$$

$$V_{GSQ} = 3 \text{ V.}$$

$$K_n = 1.5 \text{ mA/V}^2$$
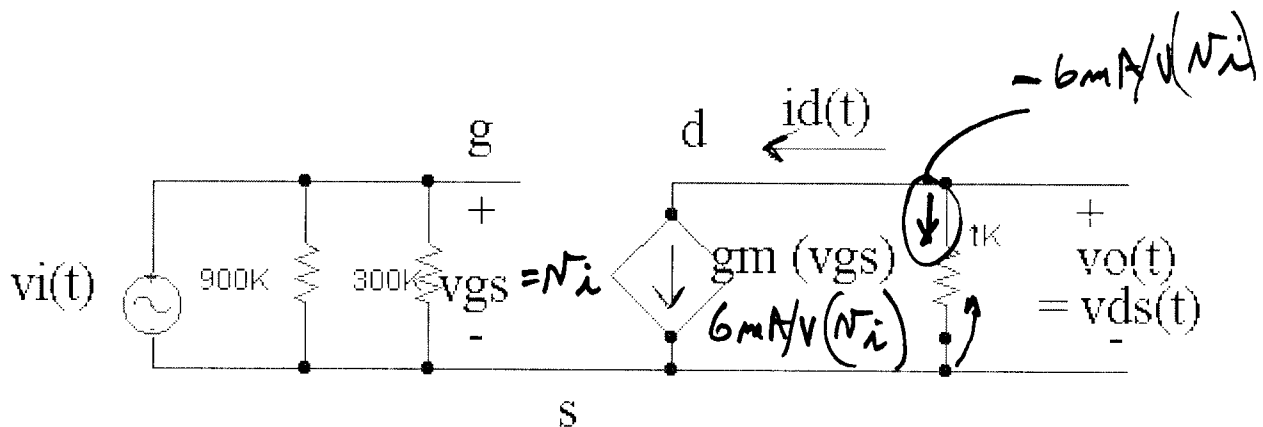
$$g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{1.5(6)} = 6 \text{ mA/V}$$



$$v_o(t) = -g_m v_{gs} R_D = -(6 \text{ mA/V}) v_{gs} (1 \text{ k})$$

$$v_o(t) = -6 v_{gs}(t)$$

$$\text{voltage gain} = \frac{v_o}{v_{gs}} = -6$$