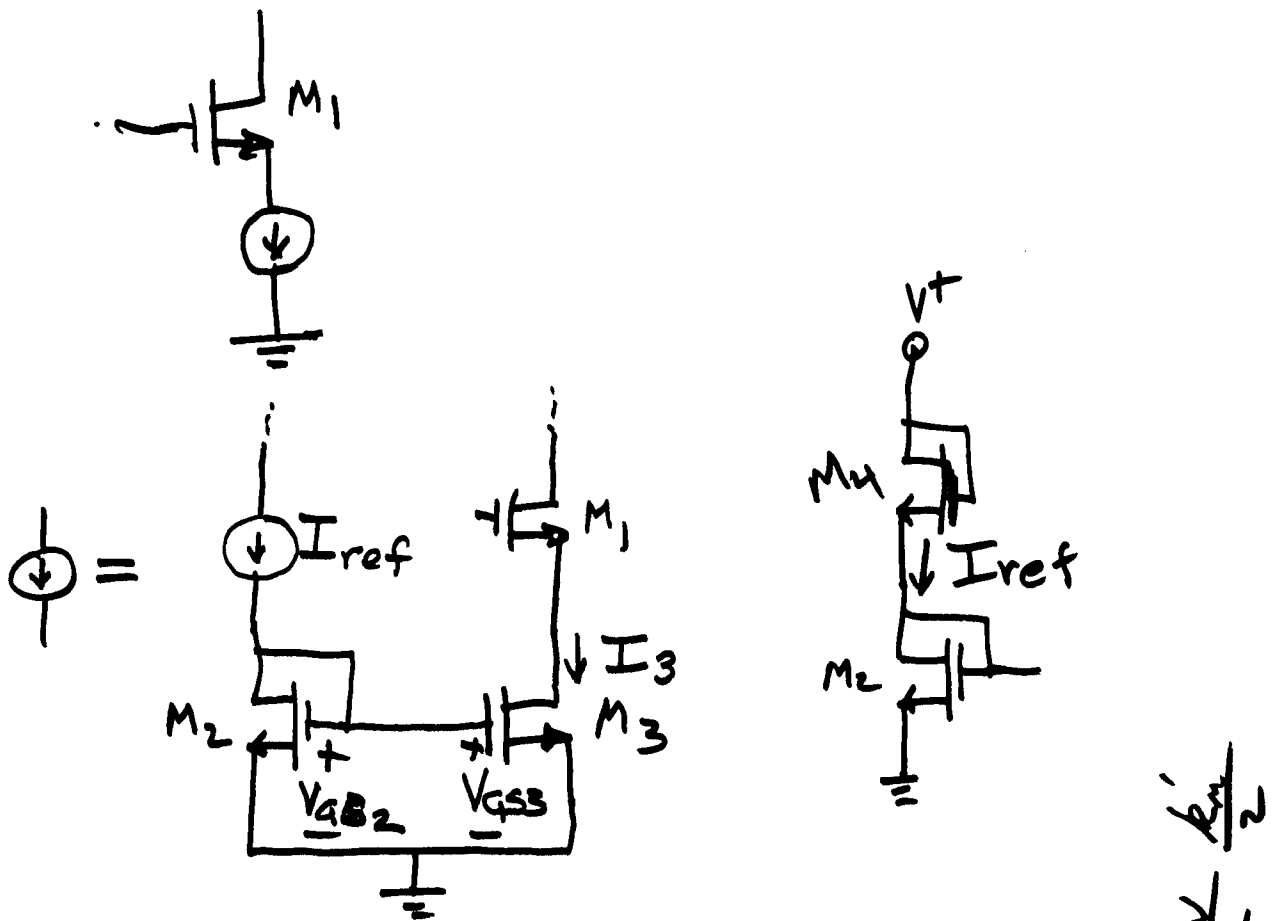


INTEGRATED-CIRCUIT AMPLIFIERS

AVOID RESISTORS

USE CURRENT SOURCE BIASING

CURRENT MIRROR



I_{ref} ESTABLISHES V_{GS2}


$$V_{GS3} = V_{GS2}$$

$$I_3 = K_{M3} (V_{GS3} - V_{TN3})^2$$

$$\frac{I_3}{I_{ref}} = \frac{K_{M3} (V_{GS3} - V_{TN3})^2}{K_{M2} (V_{GS2} - V_{TN2})^2} = \frac{K_{M3}}{K_{M2}}$$

$$= \frac{\left(\frac{W}{L}\right)_3}{\left(\frac{W}{L}\right)_2}$$

$$K_n = \frac{W}{L} \frac{k_n}{2}$$

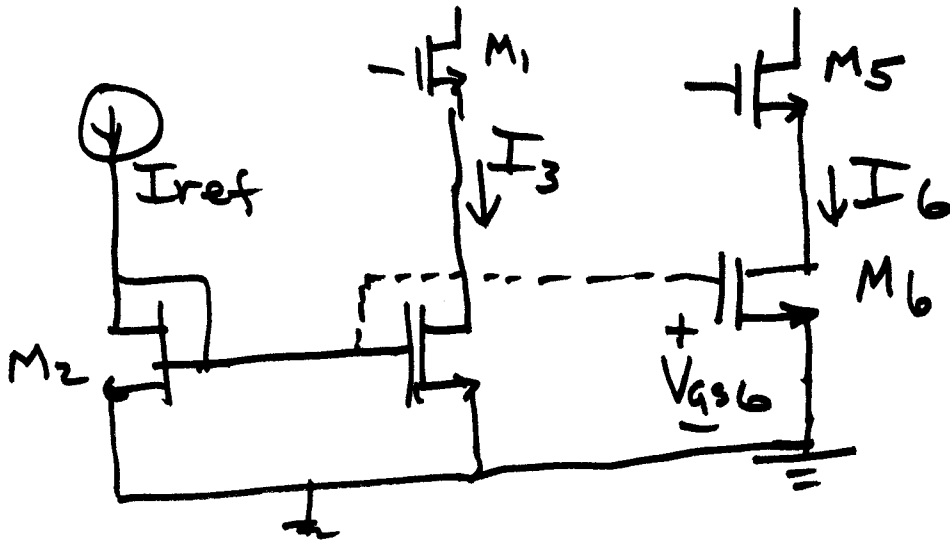

$$\frac{I_6}{I_{ref}} = \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_2}$$